

Digital Design

CS223

Lab3

Erkin Aydın

ID: 22002956

31/10/2022

Part b) of Preliminary Report:

1-to-2-Decoder module:

```
module one_to_two_dc(  
    input logic i, e,  
    output logic y1, y0;  
        assign y0 = (~i) && e;  
        assign y1 = i && e;  
endmodule
```

1-to-2-Decoder testbench:

```
module one_to_two_dc_tb();  
    logic i, e, y1, y0;  
    one_to_two_dc dc1(i, e, y1, y0);  
    initial begin  
        assign e = 0;  
        assign i = 0; #30;  
        assign i = 1; #30;  
        assign e = 1;  
        assign i = 0; #30;  
        assign i = 1; #30;  
    end  
endmodule
```

Part c) of Preliminary Report:

2-to-4-Decoder module:

```
module two_to_four_dc(
input logic i1, i0, e,
output logic y3, y2, y1, y0);
    logic d1, d0;
    one_to_two_dc dc1(i1, e, d1, d0);
    one_to_two_dc dc2(i0, d0, y1, y0);
    one_to_two_dc dc3(i0, d1, y3, y2);
endmodule
```

2-to-4-Decoder testbench:

```
module two_to_four_dc_tb();
    logic i1, i0, e;
    logic y3, y2, y1, y0;
    two_to_four_dc dc(i1, i0, e, y3, y2, y1, y0);
    initial begin
        assign e = 0;
        assign i1 = 0;
        assign i0 = 0; #90;
        assign i0 = 1; #90;
        assign i1 = 1;
        assign i0 = 0; #90;
        assign i0 = 1; #90;
        assign e = 1;
        assign i1 = 0;
```

```
assign i0 = 0; #90;
```

```
assign i0 = 1; #90;
```

```
assign i1 = 1;
```

```
assign i0 = 0; #90;
```

```
assign i0 = 1; #90;
```

```
end
```

```
endmodule
```

Part d) of Preliminary Report:

2-to-1-multiplexer module:

```
module two_to_one_mux(i1, i0, s, d);  
    input i1, i0, s;  
    output d;  
    assign d= ~s&i0 | s&i1;  
endmodule
```

Part e) of Preliminary Report:

4-to-1-multiplexer module:

```
module four_to_one_mux(i3, i2, i1, i0, s1, s0, z);  
    input i3, i2, i1, i0, s1, s0;  
    output z;  
    wire d1, d0;  
    two_to_one_mux m1(i3, i2, s0, d1); // instance1  
    two_to_one_mux m2(i1, i0, s0, d0); // instance2  
    two_to_one_mux m3(d1, d0, s1, z); // instance3  
endmodule
```

4-to-1-multiplexer testbench:

```
module four_to_one_mux_tb();  
    reg[3:0] i;  
    reg[1:0] s;  
    logic d;  
    four_to_one_mux m4(i[3], i[2], i[1], i[0], s[1], s[0], d);  
    initial begin  
        //s0 = s1 = 0;  
        //i2 = 0; i3 = 0;  
        assign s = 2'b00;  
        assign i = 4'b0000; #10;  
        assign i = 4'b0001; #10;  
        assign i = 4'b0010; #10;  
        assign i = 4'b0011; #10;  
        assign i = 4'b0100; #10;
```

```
assign i = 4'b0101; #10;
assign i = 4'b0110; #10;
assign i = 4'b0111; #10;
assign i = 4'b1000; #10
assign i = 4'b1001; #10;
assign i = 4'b1010; #10;
assign i = 4'b1011; #10;
assign i = 4'b1100; #10;
assign i = 4'b1101; #10;
assign i = 4'b1110; #10;
assign i = 4'b1111; #10;
assign s = 2'b01;
assign i = 4'b0000; #10;
assign i = 4'b0001; #10;
assign i = 4'b0010; #10;
assign i = 4'b0011; #10;
assign i = 4'b0100; #10;
assign i = 4'b0101; #10;
assign i = 4'b0110; #10;
assign i = 4'b0111; #10;
assign i = 4'b1000; #10
assign i = 4'b1001; #10;
assign i = 4'b1010; #10;
assign i = 4'b1011; #10;
assign i = 4'b1100; #10;
assign i = 4'b1101; #10;
assign i = 4'b1110; #10;
```

```
assign i = 4'b1111; #10;
assign s = 2'b10;
assign i = 4'b0000; #10;
assign i = 4'b0001; #10;
assign i = 4'b0010; #10;
assign i = 4'b0011; #10;
assign i = 4'b0100; #10;
assign i = 4'b0101; #10;
assign i = 4'b0110; #10;
assign i = 4'b0111; #10;
assign i = 4'b1000; #10;
assign i = 4'b1001; #10;
assign i = 4'b1010; #10;
assign i = 4'b1011; #10;
assign i = 4'b1100; #10;
assign i = 4'b1101; #10;
assign i = 4'b1110; #10;
assign i = 4'b1111; #10;
assign s = 2'b11;
assign i = 4'b0000; #10;
assign i = 4'b0001; #10;
assign i = 4'b0010; #10;
assign i = 4'b0011; #10;
assign i = 4'b0100; #10;
assign i = 4'b0101; #10;
assign i = 4'b0110; #10;
assign i = 4'b0111; #10;
```




```
assign i = 4'b1000; #10  
assign i = 4'b1001; #10;  
assign i = 4'b1010; #10;  
assign i = 4'b1011; #10;  
assign i = 4'b1100; #10;  
assign i = 4'b1101; #10;  
assign i = 4'b1110; #10;  
assign i = 4'b1111; #10;  
assign s= 2'b00;  
assign i = 2'b0000;
```

```
end
```

```
endmodule
```

Part f) of Preliminary Report:

8-to-1-multiplexer Block Diagram:

 

8-to-1-multiplexer module:

```
module eight_to_one_mux(  
    input logic i7, i6, i5, i4, i3, i2, i1, i0,  
    input logic s2, s1, s0,  
    output logic y);  
    logic d1, d0;  
    logic and_out1, and_out2;  
    logic s2_inv;  
    four_to_one_mux mux4_1(i3, i2, i1, i0, s1, s0, d0);  
    four_to_one_mux mux4_2(i7, i6, i5, i4, s1, s0, d1);  
    not n1(s2_inv, s2);  
    and a1(and_out1, d0, s2_inv);  
    and a2(and_out2, d1, s2);  
    or o1(y, and_out1, and_out2);  
endmodule
```

endmodule

8-to-1-multiplexer testbench:

```
module eight_to_one_mux_tb();

    reg[7:0] i;

    reg[2:0] s;

    logic d;

    eight_to_one_mux mux8(i[7], i[6], i[5], i[4], i[3], i[2], i[1], i[0], s[2], s[1], s[0], d);

    initial begin

        //i2 = 0; i3 = 0;

        assign s = 3'b000;

        assign i = 8'b00000000; #1;

        for(int j = 0; j < 255; j++) begin

            assign i = i + 8'b00000001; #1;

        end

        assign s = 3'b001;

        assign i = 8'b00000000; #1;

        for(int j = 0; j < 256; j++) begin

            assign i = i + 8'b00000001; #1;

        end

        assign s = 3'b010;

        assign i = 8'b00000000; #1;

        for(int j = 0; j < 256; j++) begin

            assign i = i + 8'b00000001; #1;

        end

        assign s = 3'b011;

        assign i = 8'b00000000; #1;
```

```

    for(int j = 0; j < 256; j++) begin
        assign i = i + 8'b000000001; #1;
    end

    assign s = 3'b100;
    assign i = 8'b000000000; #1;
    for(int j = 0; j < 256; j++) begin
        assign i = i + 8'b000000001; #1;
    end

    assign s = 3'b101;
    assign i = 8'b000000000; #1;
    for(int j = 0; j < 256; j++) begin
        assign i = i + 8'b000000001; #1;
    end

    assign s = 3'b110;
    assign i = 8'b000000000; #1;
    for(int j = 0; j < 256; j++) begin
        assign i = i + 8'b000000001; #1;
    end


    assign s = 3'b111;
    assign i = 8'b000000000; #1;
    for(int j = 0; j < 256; j++) begin
        assign i = i + 8'b000000001; #1;
    end

end
endmodule

```

Part g) of Preliminary Report:

F(A,B,C,D) Block Diagram:

 

F(A,B,C,D) module:

```
module lab_function(  
    input logic a, b, c, d,  
    output logic y);  
  
    eight_to_one_mux mux8(0, 1, 0, 1, 1, 0, 1, 0, a, b, c, y);  
endmodule
```