 


**CS223**  
**Digital Design**  
**Section 1**  
**Lab2**  
**Erkin Aydın**  
**ID: 22002956**  
**17/10/2022**

### Circuit Schematic for a half adder:



### **IC List for Circuit Schematic:**


- 1) One 7486 Quad 2-Input XOR Gate
- 2) One 7408 Quad 2-Input AND Gate

### **Pin Numbers for GND and +V for Circuit Schematic:**

7486 Quad 2-Input XOR Gate: GND-7, +5V-14

7408 Quad 2-Input AND Gate: GND-7, +5V-14
 
### Circuit Schematic for a half subtractor:



### **IC List for Circuit Schematic:**

- 1) One 7486 Quad 2-Input XOR Gate
- 2) One 7408 Quad 2-Input AND Gate
- 3) 7404 INVERTER


### **Pin Numbers for GND and +V for Circuit Schematic:**

7486 Quad 2-Input XOR Gate: GND-7, +5V-14

7408 Quad 2-Input AND Gate: GND-7, +5V-14

7404 INVERTER: GND-7, +5V-14

### Circuit Schematic for a full adder:

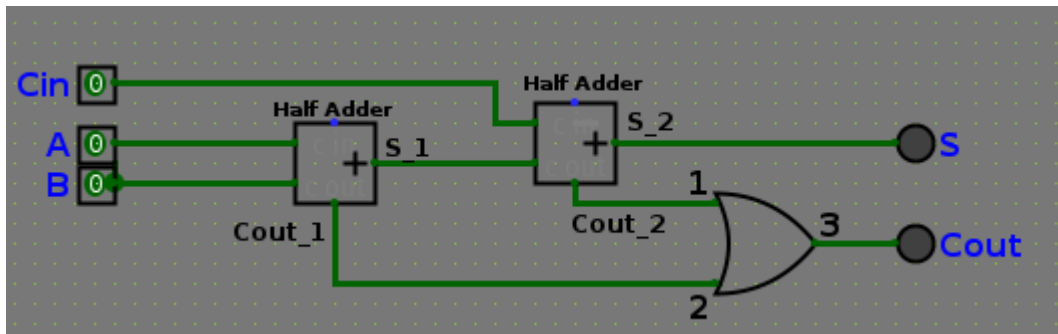

### **IC List for Circuit Schematic:**

- 1)One 7486 Quad 2-Input XOR Gate
- 2)One 7408 Quad 2-Input AND Gate
- 3)One 7432 Quad 2-Input OR Gate


### **Pin Numbers for GND and +V for Circuit Schematic:**

7486 Quad 2-Input XOR Gate: GND-7, +5V-14

7408 Quad 2-Input AND Gate: GND-7, +5V-14

7432 Quad 2-Input OR Gate: GND-7, +5V-14

### Circuit Schematic for a 2-bit adder:

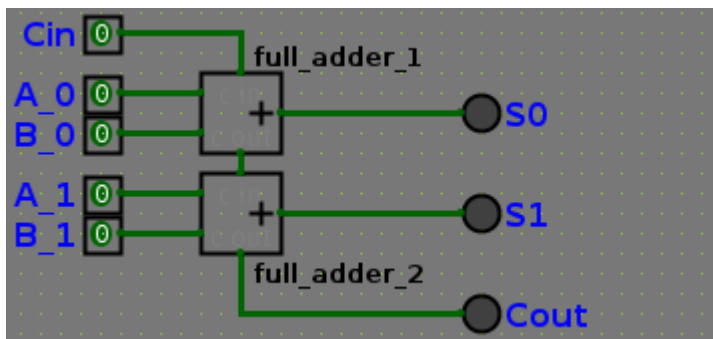

### **IC List for Circuit Schematic:**

- 1)One 7486 Quad 2-Input XOR Gate
- 2)One 7408 Quad 2-Input AND Gate
- 3)One 7432 Quad 2-Input OR Gate


### **Pin Numbers for GND and +V for Circuit Schematic:**

7486 Quad 2-Input XOR Gate: GND-7, +5V-14

7408 Quad 2-Input AND Gate: GND-7, +5V-14

7432 Quad 2-Input OR Gate: GND-7, +5V-14
 
### Circuit Schematic for a lab calculator:



### **IC List for Circuit Schematic:**

- 1)One 7486 Quad 2-Input XOR Gate
- 2)One 7408 Quad 2-Input AND Gate
- 3)One 7432 Quad 2-Input OR Gate
- 4)One 7428 Quad 2-Input NOR Gate

### **Pin Numbers for GND and +V for Circuit Schematic:**

7486 Quad 2-Input XOR Gate: GND-7, +5V-14  
7408 Quad 2-Input AND Gate: GND-7, +5V-14  
7432 Quad 2-Input OR Gate: GND-7, +5V-14  
7428 Quad 2-Input NOR Gate: GND-7, +5V-14

### Half Adder Behavioral Module:

```
//Implementation of half_adder
module half_adder(input a, b, output s, c);

    assign s = a ^ b;
    assign c = a & b;

endmodule
```

### Half Adder Testbench:

```
module half_adder_testbench();
    logic a, b, s, c;
    half_adder ha(a,b,s,c);
```

```

initial begin
assign a = 0;
assign b = 0;
#100;

assign b= 1; #100;

assign a = 1;
assign b = 0; #100;

assign b = 1; #100;

end
endmodule

```

### **Half Subtractor Behavioral Module:**

```

//Implementation of half_subtractor
module half_subtractor(input a, b, output d, bout);

    assign d = a ^ b;
    assign bout = (~a) & b;

endmodule

```

### **Half Subtractor Testbench:**

```

module half_subtractor_tb();
    logic a, b, d, bout;
    half_subtractor hs(a,b,d,bout);
    initial begin
        assign a = 0;
        assign b = 0;
        #100;

        assign b= 1; #100;

        assign a = 1;
        assign b = 0; #100;

        assign b = 1; #100;

    end
endmodule

```

```
endmodule
```

### **Full Adder Structural Module:**

```
//Implementation of full_adder
module full_adder(input a, b, cin, output s, cout);

    logic s_1, cout_1, s_2, cout_2;

    half_adder ha_1(a, b, s_1, cout_1);
    half_adder ha_2(cin, s_1, s_2, cout_2);

    assign s = s_2;
    or o( cout, cout_1, cout_2);

endmodule
```

### **Full Adder Testbench:**

```
module full_adder_tb();

    logic a, b, cin, s, cout;
    full_adder fa(a, b, cin, s, cout);

    initial begin
        assign a = 0;
        assign b = 0;
        assign cin = 0; #100;

        assign cin = 1; #100;

        assign b = 1;
        assign cin = 0; #100;

        assign cin = 1; #100;

        assign a = 1;
        assign b = 0;
        assign cin = 0; #100

        assign cin = 1; #100;

        assign b = 1;
```

```

        assign cin = 0; #100;

        assign cin = 1; #100;

    end
endmodule

```

## **2-Bit Adder Structural Module:**

```

//Implementation of two_bit_adder
module two_bit_adder(input logic [1:0]a,
                    input logic [1:0]b,
                    input logic cin,
                    output logic [1:0]s,
                    output logic cout);

    logic sum_1, sum_2, carry_1, carry_2;

    full_adder fa_1(a[0], b[0], cin, sum_1, carry_1);
    full_adder fa_2(a[1], b[1], carry_1, sum_2, carry_2);

    assign s[0] = sum_1;
    assign s[1] = sum_2;
    assign cout = carry_2;

endmodule

```

## **2-Bit Adder Testbench:**

```

module two_bit_adder_tb();

    reg [1:0]a;
    reg [1:0]b;
    logic cin;
    reg [1:0]s;
    logic cout;

    two_bit_adder two_add(a, b, cin, s, cout);

    initial begin

        assign a = 2'b00;
        assign b = 2'b00;
    end
endmodule

```

```
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b01;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b10;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b11;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
//
```

```
assign a = 2'b01;  
assign b = 2'b00;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b01;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b10;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
assign b = 2'b11;  
assign cin = 0; #20;
```

```
assign cin = 1; #20;
```

```
//
```



```
    assign a = 2'b10;
    assign b = 2'b00;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b01;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b10;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b11;
    assign cin = 0; #20;

    assign cin = 1; #20;

    //
    assign a = 2'b11;
    assign b = 2'b00;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b01;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b10;
    assign cin = 0; #20;

    assign cin = 1; #20;

    assign b = 2'b11;
    assign cin = 0; #20;

    assign cin = 1; #20;
end
endmodule
```

### **Lab Calculator Structural Module:**

```
//Implementation of lab calculator
module lab_calculator(input logic a,
                      input logic b,
                      input logic c,
                      input logic d,
                      output logic y,
                      output logic z);

    logic out_1, out_2, out_3, out_4;
    logic carry_1, bout_1;

    xor in_1(out_1, a, b);
    nand in_2(out_2, a, b);
    half_adder in_3(a, b, out_3, carry_1);
    half_subtractor in_4(a, b, out_4, bout_1);

    mux4 mux_1(out_4, out_3, out_2, out_1, c, d, y);
    mux2 mux_2(bout_1, carry_1, d, z);

endmodule
```

### **Lab Calculator Testbench:**

```
module lab_calculator_tb();

    logic a, b, c, d, y, z;

    lab_calculator lb(a, b, c, d, y, z);

    initial begin

        assign a = 0;
        assign b = 0;
        assign c = 0;
        assign d = 0; #20

        assign d = 1; #20;

        assign c = 1;
        assign d = 0; #20;
```

```
assign d = 1; #20;
```

```
//
```

```
assign a = 0;
```

```
assign b = 1;
```

```
assign c = 0;
```

```
assign d = 0; #20
```

```
assign d = 1; #20;
```

```
assign c = 1;
```

```
assign d = 0; #20;
```

```
assign d = 1; #20;
```

```
//
```

```
assign a = 1;
```

```
assign b = 0;
```

```
assign c = 0;
```

```
assign d = 0; #20
```

```
assign d = 1; #20;
```

```
assign c = 1;
```

```
assign d = 0; #20;
```

```
assign d = 1; #20;
```

```
//
```

```
assign a = 1;
```

```
assign b = 1;
```

```
assign c = 0;
```

```
assign d = 0; #20
```

```
assign d = 1; #20;
```

```
assign c = 1;
```

```
assign d = 0; #20;
```

```
assign d = 1; #20;
```

```
end
```

```
endmodule
```